

EEE F244: Micro-electronic Circuits LT-SPICE Assignment

Dt. 13.03.2018

INSTRUCTIONS

1. Make sure you comment your SPICE netlist to make it more readable.
2. Take minimum channel length as $1\mu\text{m}$. Choose convenient values of W .
3. Define your own model files for all devices.
4. All devices should operate in saturation region.
5. Some of these terms may be unfamiliar to you. It is suggested that you should look them up on the internet.
6. Take V_{DD} as 3.3V .

1. Design a Cascode amplifier with voltage gain = 100. Your amplifier should be able to amplify an input of 15mV peak-to-peak without distortion. Determine the -3dB bandwidth and Unity Gain Bandwidth.

2. Perform AC Analysis on V_{in} for the given circuit for values of V_b varying from 0 to V_{DD} and find the small signal gain. Take appropriate value of input voltage so that all transistors are in saturation region. Use $W/L = 8$ for M_2 and $W/L = 4$ for M_1 . (Circuit diagram given in Fig. 1)

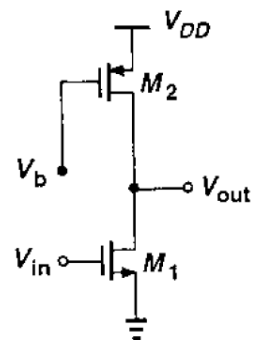


Fig. 1

3. Design a common gate amplifier with the following parameters:
Gain $\geq 40\text{dB}$
Input impedance $\leq 80\Omega$
Power dissipation $< 4\text{mW}$

4. Plot the Output vs Input Characteristics (i.e. Transfer Characteristics) for circuit in Fig. 2. Use $R_D = 2\text{K}$ and $R_S = 1\text{K}$ and $W/L = 4$ for M_1 .

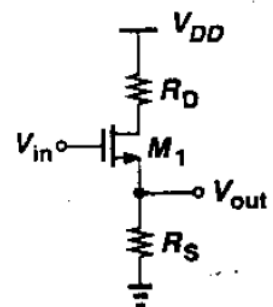


Fig. 2