



**BITS Pilani**

Pilani | Dubai | Goa | Hyderabad

# Introduction to SPICE

4/2/2018

# Contents

---

1. What is SPICE?
2. Why do we need SPICE?
3. A Simple Example using SPICE.
4. Analysis options is SPICE.

Operating point

DC Analysis

AC Analysis

Transient Analysis

5. References

# What is SPICE?



SPICE is an Acronym of

**S**imulation

**P**rogram with

**I**ntegrated

**C**ircuit

**E**mphasis

# Introduction

---

- Developed in 1970 by UCLA, Berkeley.
- Ronald Rohrer and Nagel developed CANCER program.

CANCER – Computer Analysis of Non-Linear Circuits.

- SPICE1 was derived from CANCER program.
- SPICE uses nodal analysis to solve the circuits.

# Introduction

---

- HSPICE
- PSPICE – Microsim ( first PC version)
- LT-SPIICE – Linear Technology (free version)
- NG-SPIICE (free and trusted)

# Introduction

---

- SPICE is an interpreter based language.
- The input file is called “**netlist**”
- It is also referred as “**DECK**”
- Each line in the SPICE netlist is called “**CARD**”
- The input file comes with an extension “**.cir**” / (**.sp .ckt**)
- Such file can be written using any text editor.
- Key to make any SPICE simulation is the “**model library**”
- Model libraries are **very costly**.
- Certain free libraries are also available.

Ex: Stanford PMT model files

# Structure of SPICE File

---

- Each file should have **.cir** extension

TITLE

ELEMENT DESCRIPTIONS

.MODEL STATEMENTS

ANALYSIS COMMANDS

OUTPUT COMMANDS

.END

- Single Line Comments are indicated by “\*”
- Following line comments can be indicated using “;”
- Two or more lines can be combined using “+”

# Circuit Description

---

## Elements and Representation –

**R** – Resistor     Default Unit “ Ohm”

**C** – Capacitor     Default Unit “Farad”

**L** – Inductor     Default Unit “ Henry”

- Both upper case and lower case letters are equivalent
- Element is identified by first character only.



# Circuit Description

Symbol	Prefix	Value
T	Tera	$10^{12}$
G	Giga	$10^9$
MEG	Mega	$10^6$
K	Kilo	$10^3$
F	Femto	$10^{-15}$
N	Nano	$10^{-9}$
P	Pico	$10^{-12}$
U	Micro	$10^{-6}$
M	Milli	$10^{-3}$

Table.1.List of pre-defined suffixes in SPICE

# Circuit Description Example

- Nodes is associated with a number.
- Ground is to be always denoted by “node-0”

## Examples -

R1	5	0	20K
C1	Vin	Gnd	25pF
C <sub>load</sub>	Vout	Gnd	0.30 UF
L	1	2	0.5 UH

- The data that follows valid suffix is ignored by the SPICE Simulation

# Rules for Naming in SPICE

---

- Can start with a number/alphabet.
- But once the first character is number then the following part should have only numbers. Ex. 2A is invalid node name.
- Model name can't start with a number.
- All the letters that follow a number (Value) are neglected unless they are a part of standard pre-fix table.

# Independent Sources

- V – Independent Voltage Source
- I – Independent Current Source


Name	< +ve >	<-ve>	<type>	<value>
------	---------	-------	--------	---------


Examples:

VDD	3	0	5V
-----	---	---	----

IBIAS	10	0	DC 100A
-------	----	---	---------

ISS	5	0	DC 10mA
-----	---	---	---------

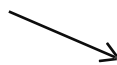
 Current flows from node-5 to node-0

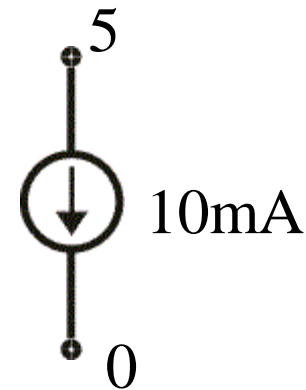

# Dependent Sources

---

- VCVS (E)– Voltage Controlled Voltage Source
- VCCS (G)– Voltage Controlled Current Source
- CCCS (F)– Current Controlled Current Source
- CCVS(H) – Current Controlled Voltage Source

# Dependent Sources

## VCVS –


$$v_5 - v_2 = 10 (v_3 - v_1)$$

E1       $\frac{5}{\downarrow}$      $\frac{2}{\downarrow}$      $\frac{3}{\downarrow}$      $\frac{1}{\downarrow}$     10     $\longrightarrow$  Gain

Output node pair      input node pair

## VCCS –


G1    2    1    (5,8)    50m

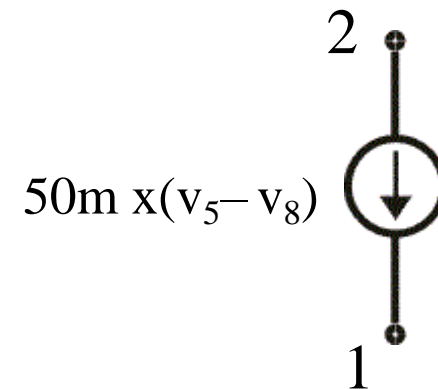

# Dependent Sources


## CCCS –

FA2    11    9    Vsupply    1.25

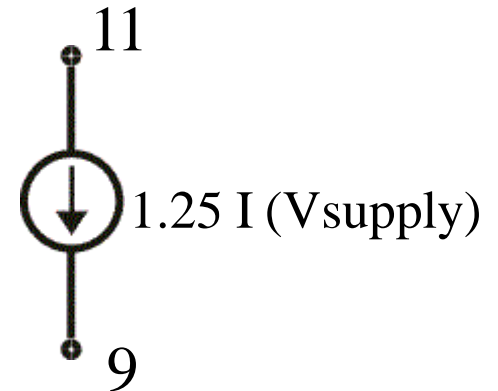


## CCVS –

Hsup    2    3    V1    10K

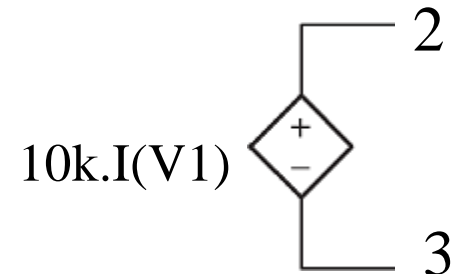

- To sense the current sometimes we need to use a “0v” voltage-source (DC) in series.

# Semiconductor Devices

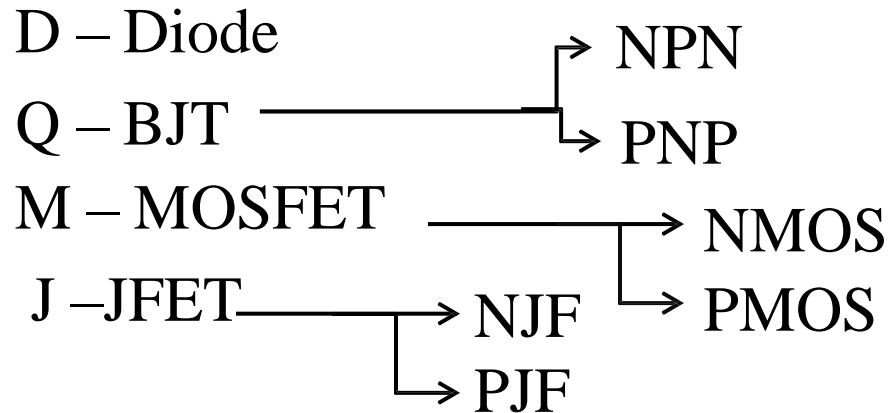

## X –SUBCIRCUITS

- All semiconductor devices can have their own model definitions and parameters.
- All the parameters need not be specified since SPICE can call default values for the unspecified values.

```
.Model ModName Type <parameters>
```



# Diode Model Declaration

---

- **Is-** Saturation Current ( 10fA)
- **N-** Emission Coefficient (1)
- **Rs-** Series Resistance ( 0 ohm)
- **Cjo-** Junction Capacitance ( 0 F)
- **TT-** Transit Time ( 0 sec)
- **BV-** Reverse Bias Breakdown Voltage ( infinite)
- **IBV-** Reverse Bias Breakdown Current ( 1 e<sup>-10</sup>)
- **VJ-** Built in Junction Potential (0.6V/0.7V)

# Diode Model Declaration

## Example :

```
.MODEL DIN4007 D  Is = 7.0276N  +
N = 1.88  Rs = 0.0345  CJO = 10p  +
TT = 0.10  BV = 1K  IBV = 50N  VJ = 0.7
```

- D1 12 15 DIN4007



# Bipolar Transistors (BJT)

---

- **BF** – Forward Active Current Gain (100)
- **Is** – Saturation Current ( .1 fA)
- **Vaf** – Early Voltage ( infinite)

Qname C B E BJT_modelName
---------------------------

# MOSFETS


Mname	D	G	S	B	ModelName	L=	W=
-------	---	---	---	---	-----------	----	----

(L & W in “m”)

- **VT0** – Threshold Voltage when  $V_{SB} = 0$
- **U0** – Mobility ( $\text{cm}^2/\text{V-s}$ )
- **KP** – Transconductance Parameter ( $\text{A}/\text{V}^2$ ) ( $2 \text{ e}^{-5}$ )
- **GAMMA** – Body Effect Parameter ( $V^{0.5}$ )
- **LAMBDA** – Channel Length Modulation ( $V^{-1}$ )
- **TOX** – Oxide Thickness (m)
- **Level no.** is the most crucial data for MOSFET modelling.

# Voltage Sources (AC)

## Sinusoidal Source:-

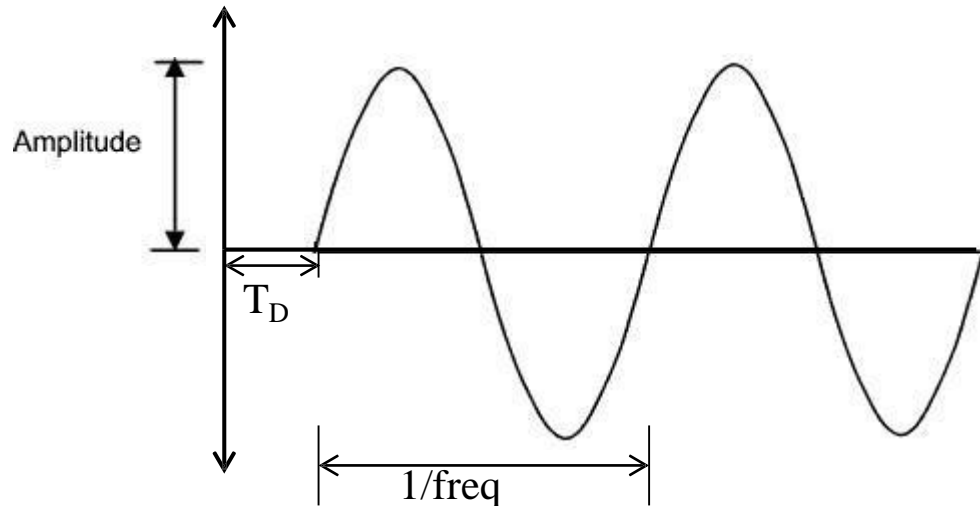

$V_{\text{sinewave}}$	N1	N2	Sin(	V0	VA	Freq	TD	$\theta$
-----------------------	----	----	------	----	----	------	----	----------

Ex:-  $V_{\text{car}}$  N1 N2 Sin(0 50m 1k)  $\Phi$ )


- Defines 1kHz sinewave of  $V_{\text{peak}} = 50\text{mV}$
- By default  $TD=0$ ,  $\theta=0$ ,  $\Phi=0$
- $\theta$  is for exponential damping sinewave (damping factor)

# Piece-Wise Linear (PWL)


Vname
N1
N2
PWL
(T1
V1
T2
V2 ...)

- $T_i - V_i$  = Voltage Value at a given time  $T_i$

V1	1	2	PWL	+
0	0	50	0	+
100	5	300	5V	+
350	0	500	0V	550
			7V	

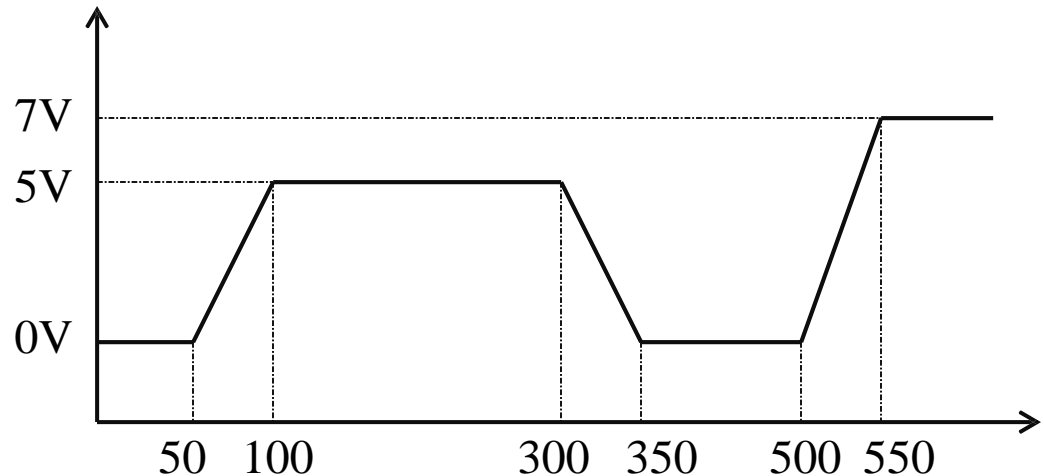

# Pulse Waveform (clock waveform)

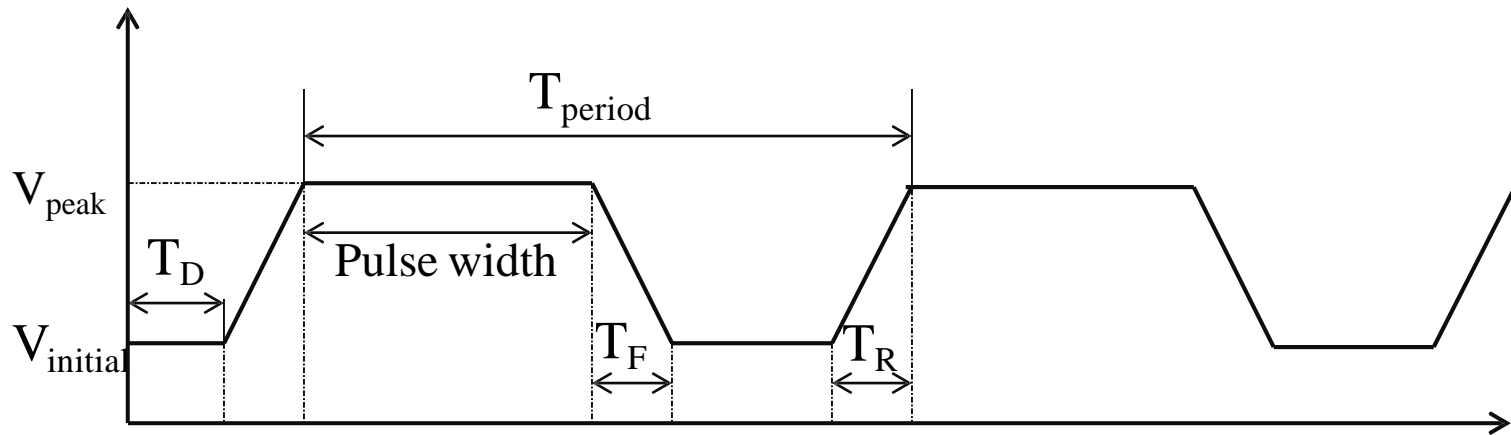

Vpulse	N1	N2	Pulse (V1	V2	TD	TR	TF	PW	PER)
--------	----	----	-----------	----	----	----	----	----	------

Ex:- Square Waveform 33% Duty Cycle 10kHz

Vsquare N1 N2 Pulse (0 5 10p 10p 10p 33u 0.1m )

- Specify Rise Time and Fall Time in ps if they are of no specific importance.

## Sub-Circuits ( letter X is reserved for them )

---

```
.SUBCKT subckt_name nodes_externally
```

Element Statements

```
.ENDS subckt_name
```

- Node 0 still remains ground
- Node name can't be node 0
- Internal node names are always local
- Opamps are always modelled as subcircuits



# Control Statements

---

## **DC Operating Point - .op**

- Voltages at the nodes
- Current in each voltage source
- Operating point for each element
- Automatically done before AC or Transient Analysis

# Control Statements

---

## DC Analysis - .dc

- Better understood as dc sweep analysis
- Can be done on any ( one or more ) independent sources

`.DC source_name Start Stop Step`

Ex : `.DC Vapplied 0 1.2 .01`

- Nesting of dc sweep is allowed and done often

Ex : `.DC Vds 0 3.3 0.1 Vgs 0 1.8 0.6`

# Control Statements

---

## Transient Analysis - .tran

- Time varying signals used to plot Vs time
- Internally operating points are always calculated

`.tran    tstep    tstop    tstart (default zero)`

Note. Used in general to observe the time response of the circuits.

# Control Statements

## AC analysis - .ac

- Used to perform frequency analysis
- Filters , Amplifiers and Resonant Circuits

.ac	<u>mode</u>	<u>np</u>	fstart(Hz)	fstop(Hz)
-----	-------------	-----------	------------	-----------

lin/dec/oct      no of points per dec/oct

Ex:-      .ac   dec   10   1   10k

- Plots frequency response from 1 Hz to 10Khz with each decade having 10 sample points.
- In general decade sweep is used for frequency response.

# Control Statements

---

## Transfer function - .tf

- Plots the transfer function ( small signal )

```
.tf output_variable source
```

- Can be used to calculate the thevenin equivalent
- Output also contains : a) Resistance with respective input source  
b) Resistance with respective output source

Ex:- .tf vout vin

# Control Statements

---

## Sensitivity Analysis - .sens

- Plots the sensitivity of the variable with respect to every circuit parameter ( small signal values )

`.sens variable`

- Can be used to calculate power supply dependencies, resistance tolerance etc

## Additional Resources

---

1. <https://vision.lakeheadu.ca/eng4136/spice/index.html>
  2. <http://www.ecircuitcenter.com/SPICEsummary.htm>
  3. *List of Teaching Assistants* -  
<https://docs.google.com/spreadsheets/d/1mZVkgLm2miW1pYADgRn2tXi6tSlGk4C-xHr2PJEK3Ss/edit?usp=sharing>
-